

---

# Nanoelectronic Circuit Design

## Design, simulation and analysis in SPICE


Ramon Canal

Dept. Arquitectura de Computadors (DAC)

UPC-Barcelona Tech

Based on the slides made by Prof. Enric Pastor (DAC, UPC)

# The Design Problem

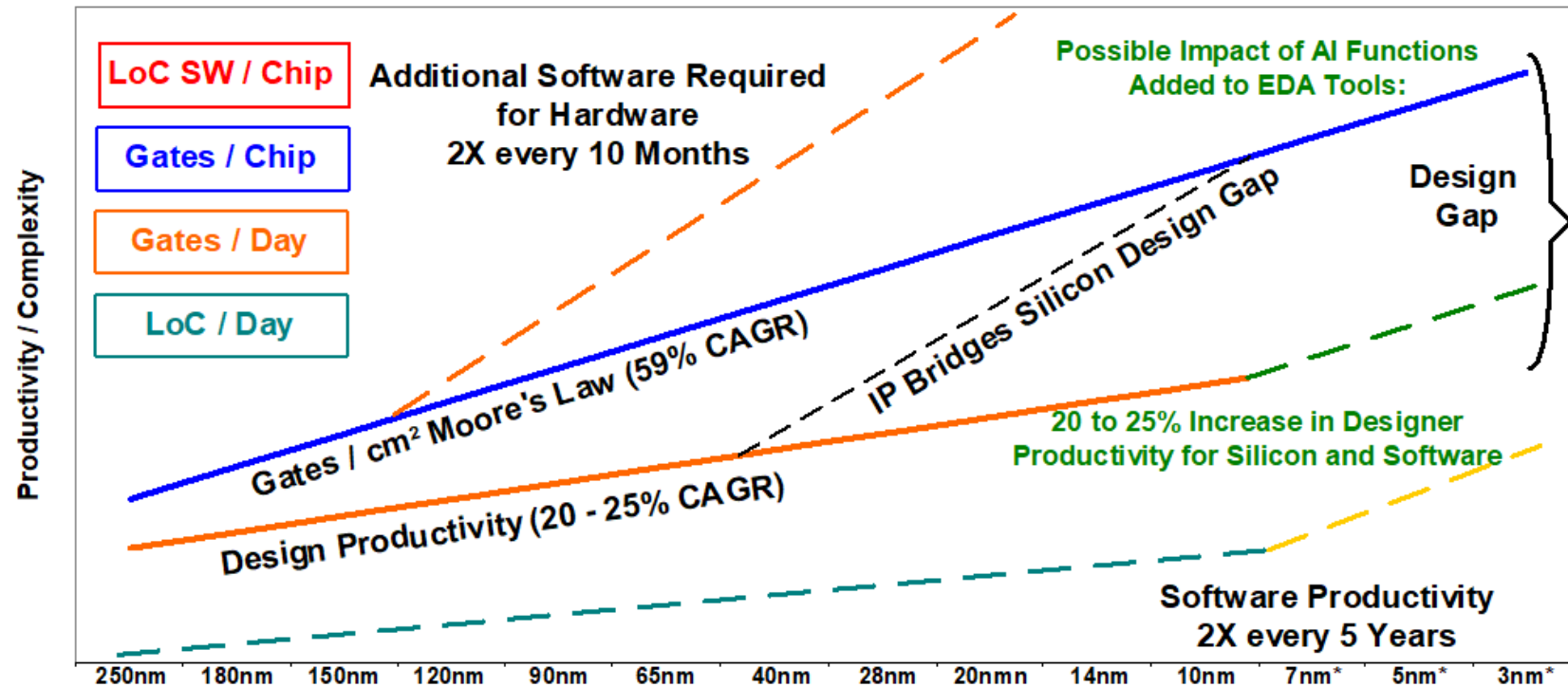


Source: Semico Research Corp. June, 2018

\*Note: Further explanation of the graph above is provided in Semico's report *Silicon and Software Design Costs* (SC103-18).



**A growing gap between design complexity and design productivity**

# Design Methodology


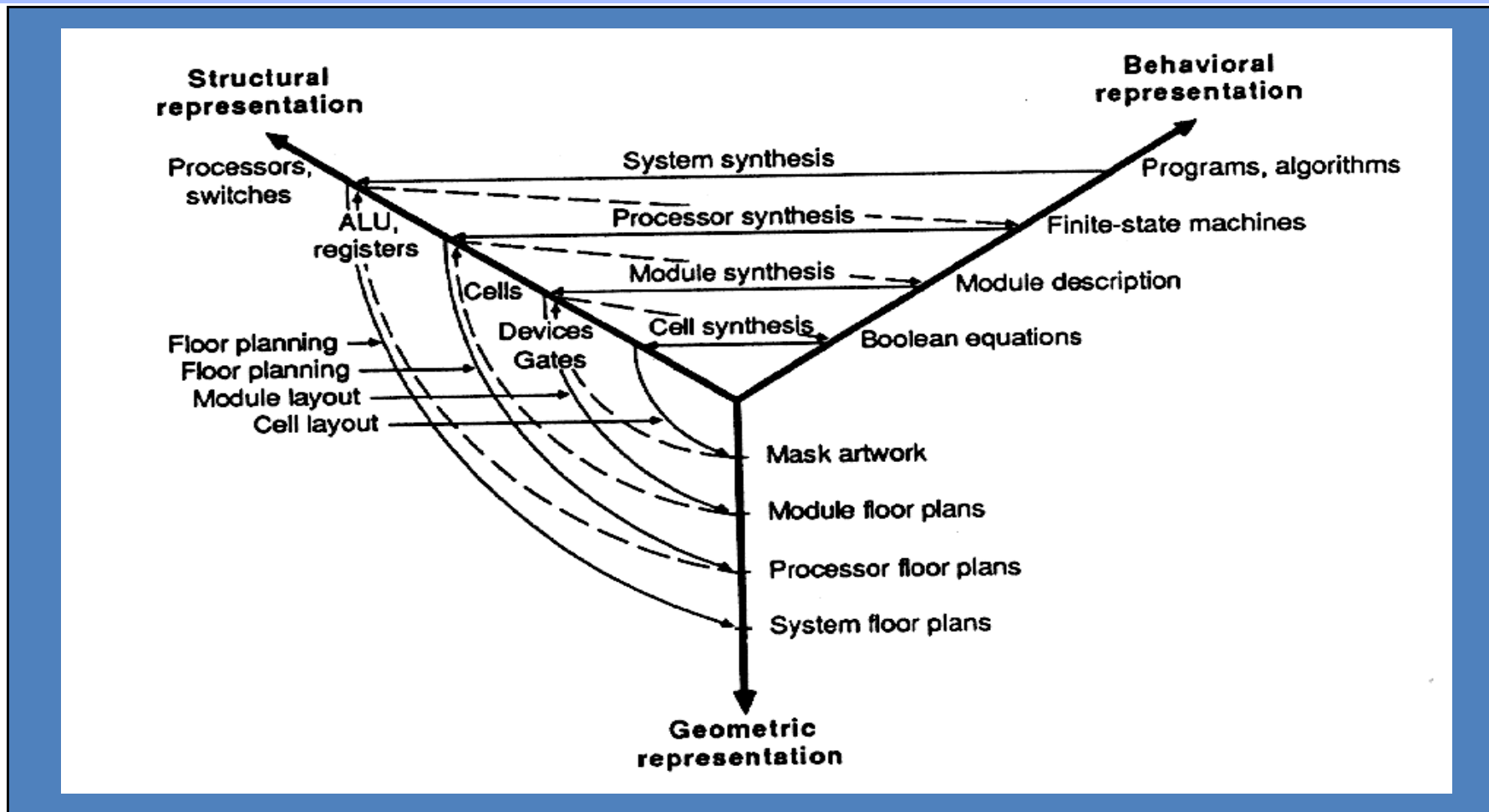


- Design process traverses iteratively between three abstractions: behavior, structure, and geometry
- More and more automation for each of these steps

# Tools across Design Space

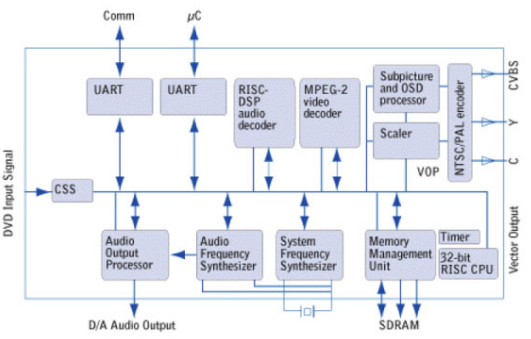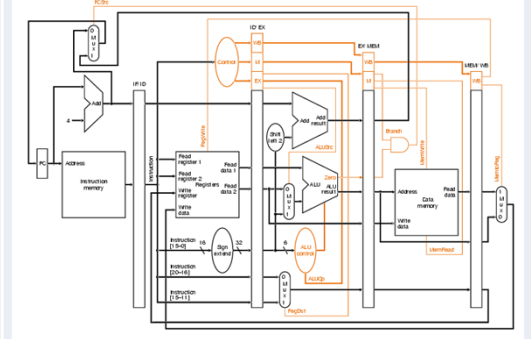Design Level		Tools	Simulation Type
<p>CPU/SoC</p>		<p>Custom built in HLL (SimpleScalar, Gem5, Marssx86, Multi2Sim, GPGPU, ...)</p> <p>Input: Block timing, benchmarks [extra power/temperature models (i.e. Watch, McPAT, CACTI, or self-made)]</p>	<p>Functional simulation</p> <p>Output: performance characterization</p>
<p>Circuit Level (functional [+ timing])</p> <p><i>Bigger blocks, whole CPU</i></p>		<p>VHDL, verilog</p> <p>Input: circuit [+ circuit timing]</p>	<p>Logic</p> <p>Output: Behavior, Results [timing].</p>

# Tools across Design Space (cont.)

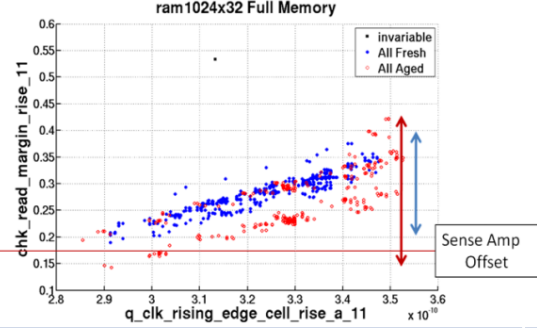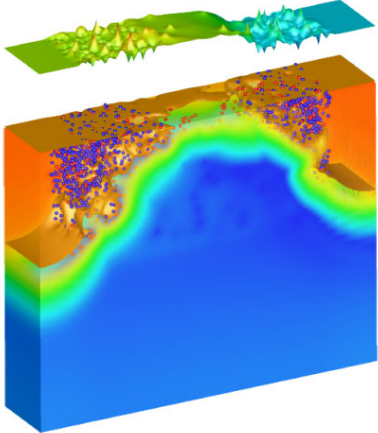Design Level		Tools	Simulation Type
Circuit Level (analog)  <i>Usually small blocks</i>		SPICE  Input: Compact Model	Electrical simulation  Output: characterization (delay, power, etc.)
Device (i.e. Transistor)		TCAD, atomistic simulators or similar  Input: physical description of materials	Particle Physics  Output: Compact Model

# Content

---


- Overview of SPICE
- SPICE Description:
  - Nodes
  - Basic components
  - Transistors: dimensions and capacity
  - Modular Design
  - Definition of inputs
  - Power measurement
  - Buses
- Technology: BSIM 28nm
- Example: an inverter, Brent-Kung 32 bit adder

# Content

---

- Simulation Program with Integrated Circuit Emphasis
- General purpose analog circuit simulator
- Used in IC and board-level design for check of integrity of circuit designs and prediction of circuit behavior
- Developed at Electronics Research Laboratory of the University of California, Berkeley (1973)
- SPICE simulation is industry-standard for verification of circuit operation at transistor level before manufacturing

# Modeling Technologies

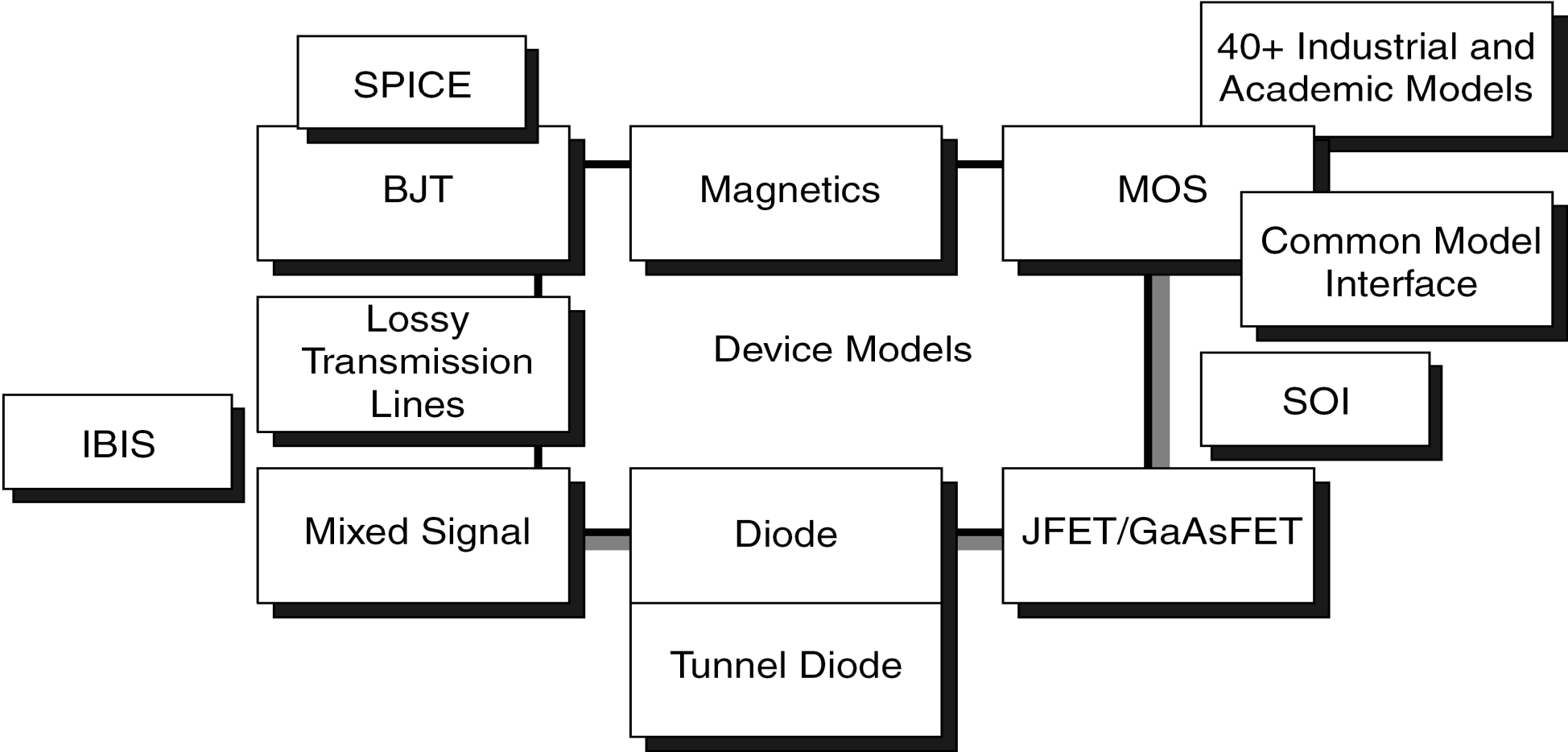

# SPICE: electrical simulator


---

- SPICE supports several types of components:
  - Resistance, capacitors, voltage sources...
  - Transistors NMOS, PMOS
  - Buses
  - Modular description
- Behavior is simulated as nonlinear differential equations:
  - Simple models for resistances and capacitances
  - Several different models for transistors
- SPICE simulates by discretizing time
  - Solving by implicit integration methods, Newton's method and sparse matrix techniques
  - May not converge or reduce simulation intervals
  - No convergence may mean a wrong design

# SPICE description:
 
# Nodes





- SPICE analyzes networks of nodes:
  - Each node can be connected to other ones through components
  - Each node has a unique name or number
  - Nodes do not have a special direction (current)
  - Special nodes are **1** (Vdd) and **0** (Gnd)



# SPICE description:
    
# Components

- The first character of the description defines the component type
- Most common components are:
  - Resistance **R**id node1 node2 value(*ohms*)
  - Capacitance **C**id node1 node2 value (*farads*)
  - Voltage source **V**id node1 node2 value (*volts*)
  - Current source **I**id node1 node2 value (*amperes*)



# SPICE description:

# Components

---

- Other components:

– Diode **D**id

– Linear Inductor **L**id

– JFET or MESFET **J**id

– Bipolar Transistor **Q**id

– Transmission Line **T**id, **U**id, **W**id

– Subcircuit **X**id <subcircuit parameters>

# SPICE description:


# Transistors

- We can model a plethora of devices
- We will concentrate on MOS type transistors:

**M***id*      *nodeD* *nodeG* *nodeS* *nodeB* *type*

- Description:

 - ***nodeD***: drain                      ***nodeG***: gate
- ***nodeS***: source                      ***nodeB***: bulk
- **type**:NMOS / PMOS




# SPICE description:
 
# Transistors

- Additional parameters:
  - $W$ : channel width       $L$ : channel length
  - $PD$  /  $PS$ : perimeter of the Drain/Source
  - $AD$  /  $AS$ : Area of the Drain/Source


$Mid$   $nD$   $nG$   $nS$   $nB$   $type$   $W=$   $L=$   $PD=$   $AD=$   $PS=$   $AS=$



# SPICE description:

 
# Transistors

- How do we compute the perimeters and areas in a transistor?



# SPICE description:


# Transistors

 

# SPICE description:
 
# Transistors

- L and W determine the performance of the transistor:
  - Resistance  $\sim L/W$
  - L: higher resistance
  - W: smaller resistance
- PMOS transistor:
  - Smaller current than NMOS
  - 2-3 times slower



# SPICE description:

# Modules

---

- Subcircuit definition:

```
.SUBCKT Name NodeList
```

```
*Definition of content
```

```
.ENDS Name
```

- Highly recommended:

```
NodeList: InputList OutputList 1 (Vdd) 0 (Gnd)
```

- Subcircuit instantiation:

```
Xid NodeList Name
```

# SPICE description:


# Multiple Modules

- The M (multiply) parameter:

\* Definition *Val* copies of *SubcircuitName* connected in parallel

*Xid NodeList SubcircuitName M=Val*

 - Useful for large parallel structures, such as:
  - Memories (register file, caches, etc.)



# SPICE description:

# Inputs

- Definition of inputs:
  - Signal wave (chronogram)
  - List of points in the wave (time-value pairs)
  - Lineal interpolation between consecutive points

**Vnode Node 0 pw1 (*Time1 Value1 Time2 Value2 ...*)**


- Intricacies:
  - Define the value for initial (0) time
  - $\text{Time}_x < \text{Time}_{x+1}$  (no 0-delay transitions allowed!)
  - Each edge needs 2 points to define the transition slope

# SPICE description:

# Inputs

 - Example:

```
Vnode Node 0  pw1 (  0ns  5    3ns  0
+                    7ns  5    7.5ns 0
+                    11ns 0    11.5ns 5
+                    14.5ns 5  15ns  0)
```



# SPICE description:

---

# Pulses

- Description of periodic signals:
  - **V1** Initial value
  - **V2** Value during the pulse
  - **TD** Initial delay of the pulse
  - **TR** Raise time
  - **TF** Fall time
  - **PW** Pulse width
  - **PER** Pulse period


**Vnode Node 0 PULSE (V1 V2 TD TR TF PW PER)**

# SPICE description:

# Pulses

 - Example:

```
Vnode Node 0 PULSE ( 0      5  
+           3ns  1ns  1ns  4ns  
+           12ns)
```



# SPICE description

# Power Delivery


- Voltage source:
  - Defines the electrical values for *Vdd* and *Gnd*
  - Same common values for all the system.

\* 5v between vdd (node 1) and gnd (node 0)

```
VCC 1 0 DC 5V
```

```
XSUM A15 A14 ... A2 A1 A0 B15 B14 ... B2 B1 B0
```

```
+ S15 S14 ... S2 S1 S0 1 0 sum16
```

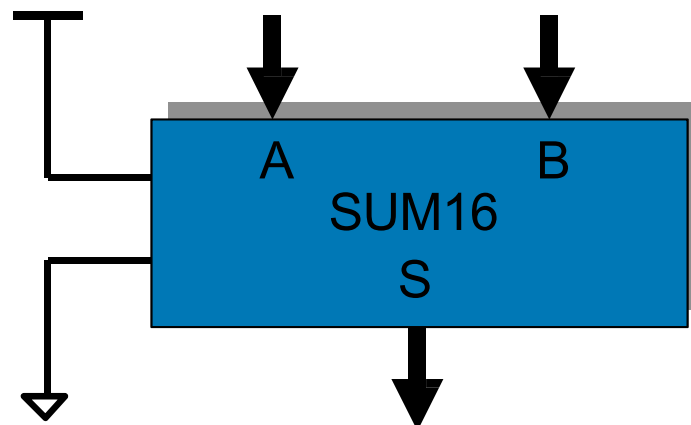


# SPICE description:
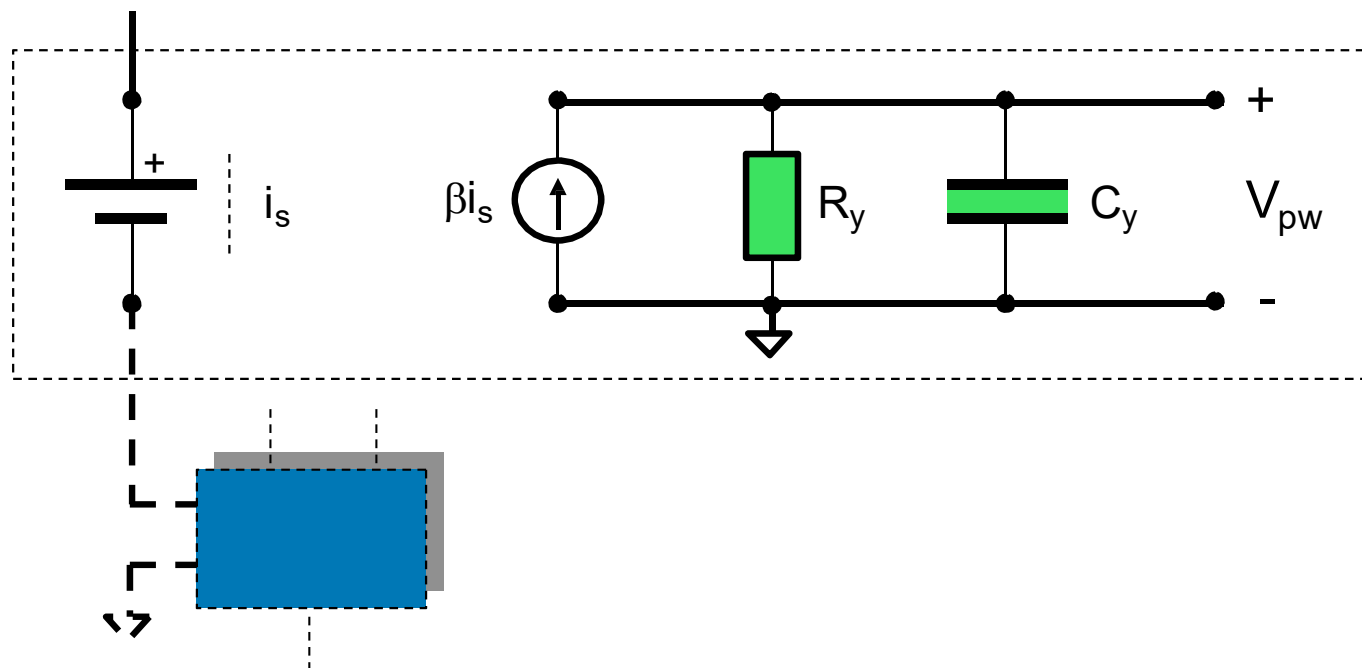
# Power Delivery

- Voltage source:
  - Current sensor: current + total accumulated power


```
XPS Vsupp Vpw 1 0 Pmeter
XSUM A15 A14 ... A2 A1 A0 B15 B14 ... B2 B1 B0
+ S15 S14 ... S2 S1 S0 Vsupp 0 sum16
```



# SPICE description:
 
# Interconnects


- Data transmission:
  - A conductor over a substrate
- Communication models:
  - Transmission line analysis
  - Lumped-element analysis



# SPICE description:
 
# Transmission line


- Segment analysis:
  - Resistance ( $R_{dz}$ ), capacity ( $C_{dz}$ ), inductance ( $L_{dz}$ ) and leakage ( $G_{dz}$ ) per unit of length (i.e. nanometer) in the connection.



# SPICE description:
 
# Transmission line


- Channel with losses:
  - Resistance ( $R_{dz}$ ) and leakage ( $G_{dz}$ ) cause a reduction of current and a drop of voltage.



# SPICE description:
 
# Transmission line


- Channel without losses:
  - We need to model just capacity ( $C_{dz}$ ) and inductance ( $L_{dz}$ ). This affects *only* delay.



# SPICE description:
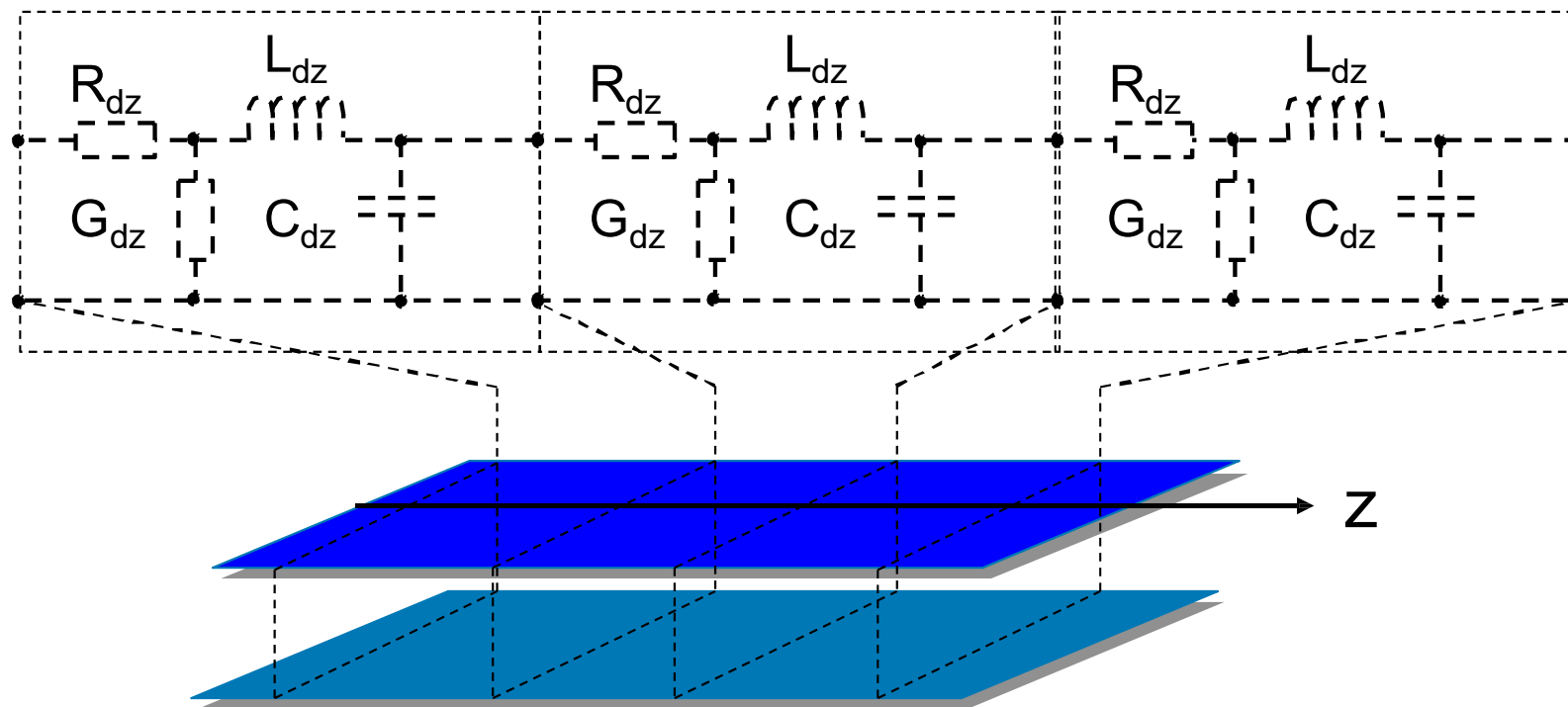
# Lumped-Element


- Simulation of a channel with losses:
  - Use multiple transmission elements



# SPICE description:

 
# Lumped-Element

- Simulation of a channel without losses :
  - Use multiple transmission elements



# SPICE description:

0.35 $\mu$ /0.5 $\mu$  Technology

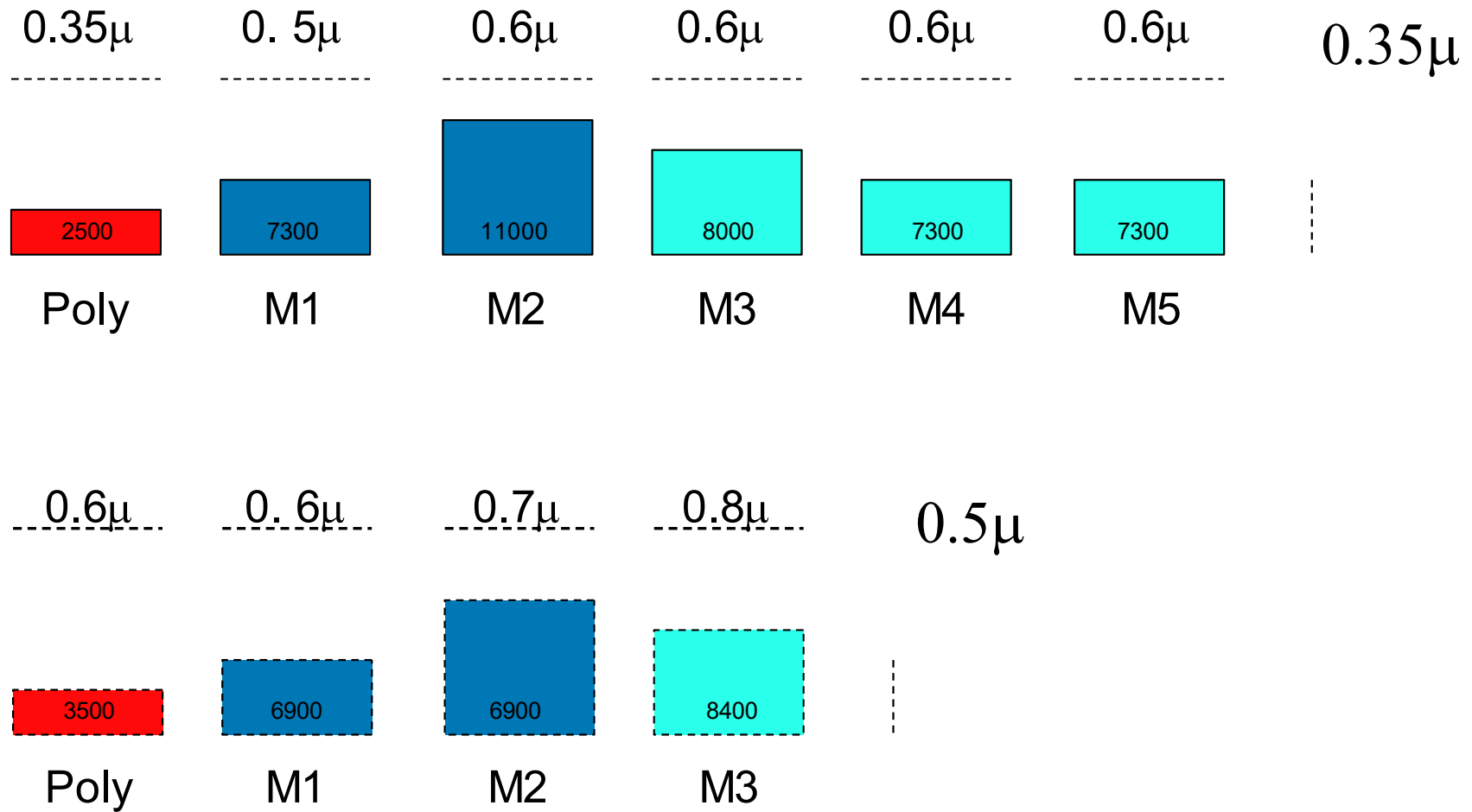

# SPICE description:

0.35 $\mu$  Technology

---

- Resistance parameters:

Poly Sheet R	10 - 30 $\Omega/\bullet$
N+ Sheet R	10 - 30 $\Omega/\bullet$
P+ Sheet R	10 - 30 $\Omega/\bullet$
M1-M5 Sheet R	35 - <b>55</b> - 75 m $\Omega/\bullet$
High poly Sheet R	800 - <b>1000</b> - 1200 m $\Omega/\bullet$
Contact R	2 - 15 $\Omega/\text{cnt}$
Via R	1 - 3 $\Omega/\text{cnt}$

# SPICE description:

0.35 $\mu$  Technology

---

- Capacity parameters:

M1 to DIFF	<b>0.036</b> fF/ $\mu\text{m}^2$
M1 to POLY	<b>0.047</b> fF/ $\mu\text{m}^2$
M1 to SUB	<b>0.033</b> fF/ $\mu\text{m}^2$
M2 to SUB	<b>0.012</b> fF/ $\mu\text{m}^2$
M3 to SUB	<b>0.008</b> fF/ $\mu\text{m}^2$
M4 to SUB	<b>0.005</b> fF/ $\mu\text{m}^2$
M5 to SUB	<b>0.004</b> fF/ $\mu\text{m}^2$
POLY to SUB	<b>0.126</b> fF/ $\mu\text{m}^2$
POLY	<b>4.93</b> fF/ $\mu\text{m}^2$

# SPICE description:

0.35 $\mu$ /0.5 $\mu$  Technology

---

- Resistance parameters:

Poly Sheet R	10 $\Omega/\bullet$	30 $\Omega/\bullet$
N+ Sheet R	10 $\Omega/\bullet$	90 $\Omega/\bullet$
P+ Sheet R	10 $\Omega/\bullet$	115 $\Omega/\bullet$
M1-M5 Sheet R	55 m $\Omega/\bullet$	85 - 55 m $\Omega/\bullet$
High poly Sheet R	1000 m $\Omega/\bullet$	- - - -
Contact R	2 - 15 $\Omega/\text{cnt}$	40 - 80 $\Omega/\text{cnt}$
Via R	1 - 3 $\Omega/\text{cnt}$	1 - 3 $\Omega/\text{cnt}$

# SPICE description:

0.35 $\mu$ /0.5 $\mu$  Technology

---

- Capacity parameters:

M1 to DIFF	<b>0.036</b> fF/ $\mu\text{m}^2$	<b>0.031</b> fF/ $\mu\text{m}^2$
M1 to POLY	<b>0.047</b> fF/ $\mu\text{m}^2$	<b>0.049</b> fF/ $\mu\text{m}^2$
M1 to SUB	<b>0.033</b> fF/ $\mu\text{m}^2$	<b>0.031</b> fF/ $\mu\text{m}^2$
M2 to SUB	<b>0.012</b> fF/ $\mu\text{m}^2$	<b>0.011</b> fF/ $\mu\text{m}^2$
M3 to SUB	<b>0.008</b> fF/ $\mu\text{m}^2$	<b>0.007</b> fF/ $\mu\text{m}^2$
M4 to SUB	<b>0.005</b> fF/ $\mu\text{m}^2$	- - - -
M5 to SUB	<b>0.004</b> fF/ $\mu\text{m}^2$	- - - -
POLY to SUB	<b>0.126</b> fF/ $\mu\text{m}^2$	<b>0.12</b> fF/ $\mu\text{m}^2$
POLY	<b>4.93</b> fF/ $\mu\text{m}^2$	<b>2.56</b> fF/ $\mu\text{m}^2$

# Numbers

---

- Numbers can be
  - Integer
  - Floating point
  - Floating point with integer exponent
  - Integer or floating point with one scale factor
- Numbers can use
  - Exponential format
  - Engineering key letter format
  - Not both (1e-12 or 1p, but not 1e-6u)

Prefix	Scale Factor	Multiplying Factor
Tera	T	1e+12
Giga	G	1e+9
Mega	MEG or X	1e+6
Kilo	K	1e+3
Milli	M	1e-3
Micro	u	1e-6
Nano	n	1e-9
Pico	p	1e-12
Femto	f	1e-15
Atto	a	1e-18

# Comments

---

\* \*\*\*\* Parameters \*\*\*\*

Comments:

- First letter of line is **asterisk (\*)** → **whole line** is comment
- **Dollar sign (\$)** anywhere on the line → **text after** is comment

For example:

```
* <comment_on_a_line_by_itself>
```

-or-

```
<HSPICE_statement> $ <comment_following_HSPICE_input>
```

Comment statements can be placed anywhere in circuit description

# Parameters and Expressions

---

```
.param Wn=2u L=0.6u
```

```
.param Wp='2*Wn'
```

- Definition of netlist parameters
- Parameter can be defined with expressions
- Definition can occur after use in elements
- Parameter names must begin with alphabetic character
- At redefinition last parameter's definition is used
- Expressions cannot exceed 1024 characters

# Transient analysis with “Sweeps”

---

- Transient analysis simulates circuit in a specific time
- Simple syntax:
  - `.TRAN <Tstep> <Tstop>`
  - `<Tstep>`: time step
  - `<Tstop>`: End time (duration) of simulation
- Also more complex commands possible

```
.TRAN 200P 20N SWEEP TEMP -55 75 10
```

- *Time step: 200 ps, Duration: 20 ns*
- *Multipoint simulation: temperature is swept from -55 to 70°C by 10°C steps*

# PLOT statement

---

```
.plot ov1 [ov2 ... ovN]
```

- Generate a plot for including all variables ov1...ovN
- oVx can be:
  - $V(n)$ : voltage at node n.
  - $V(n1<,n2>)$ : voltage between the n1 and n2 nodes.
  - $Vn(d1)$ : voltage at nth terminal of the d1 device.
  - $In(d1)$ : current into nth terminal of the d1 device.
  - 'expression': expression, involving the plot variables above

# Measure statement

---

**.MEASURE <ana\_type> <param\_name> <meas\_mode>**

**<param\_name>**: Parameter name

**<Meas\_mode>** Measurement mode, e.g.:

- Rise, fall, and delay
- Find-when
- Average, RMS, min, max, and peak-to-peak
- Integral evaluation
- Derivative evaluation


**.MEASURE tran vin AVG V(nt1) from=0 to=1n**

- Parameter name: **vin**
- Measurement type: **Average**
- Value: **Voltage of net n1**

# Example: inverter

---


- Schematic and gate:

 

# Example: inverter (@28nm)
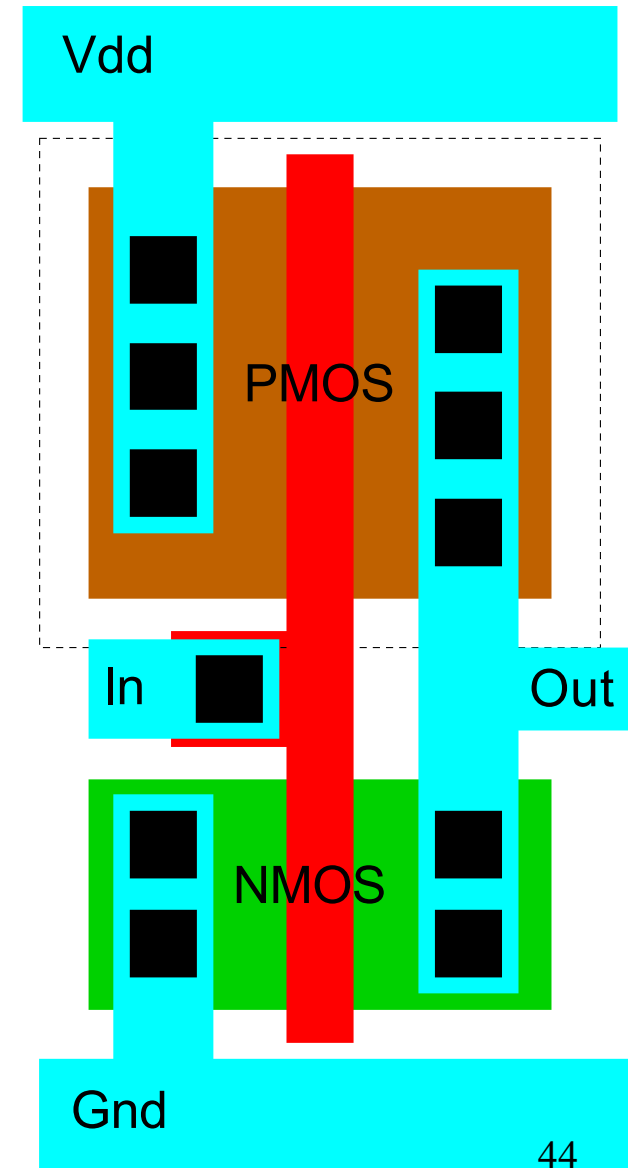
# Layout


- L/W values:
  - $L_p = 56n$  ( $2\lambda$ )  $W_p = 448n$  ( $16\lambda$ )
  - $L_n = 56n$  ( $2\lambda$ )  $W_n = 224n$  ( $8\lambda$ )
- Areas: ( $N=6\lambda$ )
  - $AD_p = AS_p = 448n * 6(28n) = 75.3f$
  - $AD_n = AS_n = 224n * 6(28n) = 37.6f$
- Perimeters:
  - $PD_p = PS_p = 2(448n + 168n) = 1.23u$
  - $PD_n = PS_n = 2(224n + 168n) = 784n$



# Example: inverter

---

- Schematic and gate:

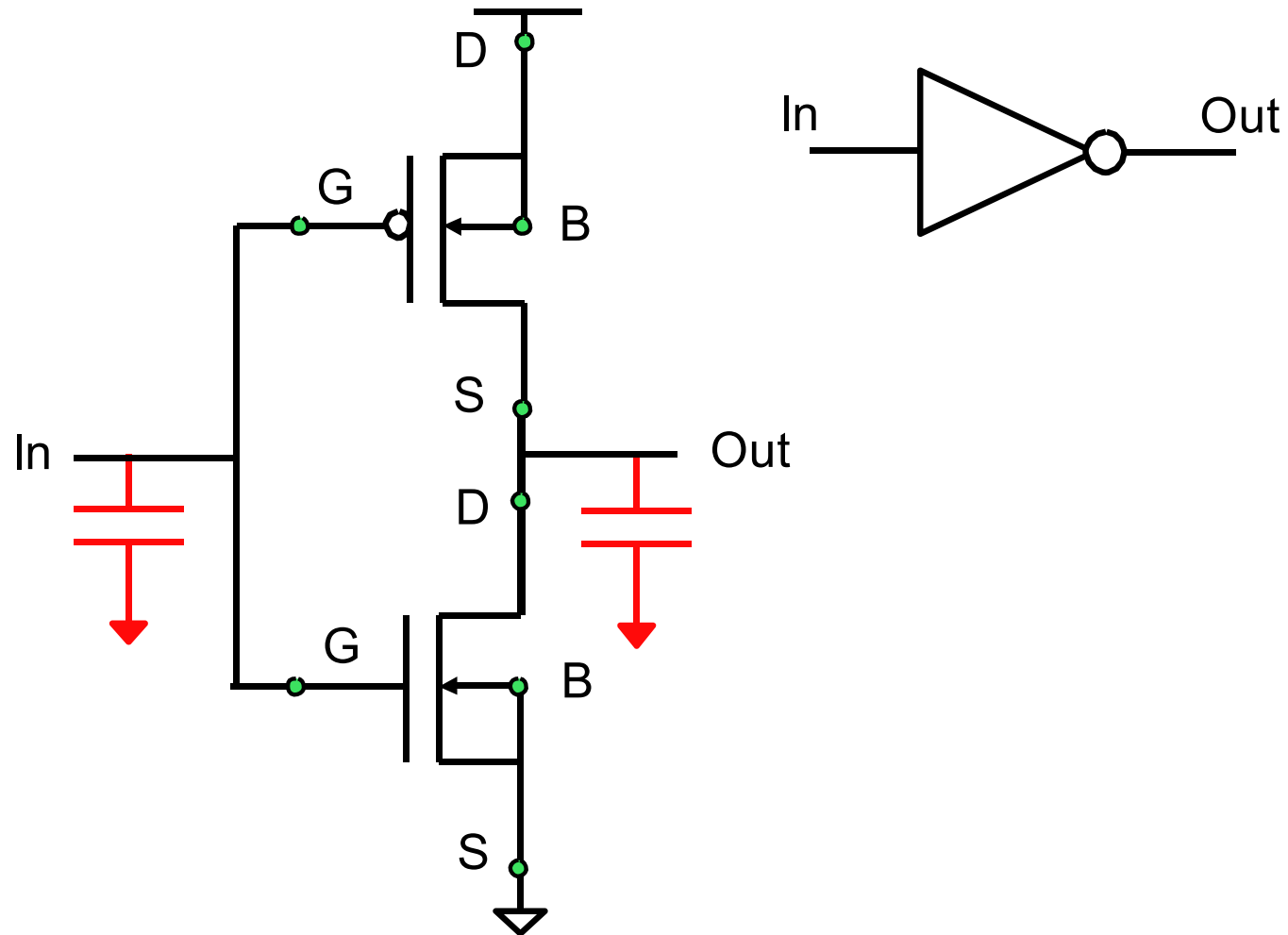

# Example: inverter

# SPICE Model

---

\*Definition of the inverter subcircuit In Out

```
.SUBCKT inv In Out 1 0
```

\*Pull-up

```
M1 1 In Out 1 tp L=56n W=448n AS=75.3f AD=75.3f PS=1.23u PD=1.23u
```

\*Pull-down

```
M2 Out In 0 0 tn L=56n W=224n AS=37.6f AD=37.6f PS= 784n PD=784n
```

\*Optional: metal input/output capacitances

```
C1 In 0 24P
```


```
C2 Out 0 10P
```

```
.ENDS inv
```

# Example: inverter
 
# Layout


- Input metal capacitance:
  - Area: ? Need layout
  -
- Input poly capacitance:
  - Area: ? Need layout
  -
- Output metal capacitance:
  - Area: ? Need layout
  -



# Example: inverter
 
# Layout

- Gate capacitance:
  - Area: automatic
- Diffusion capacitance:
  - Area: automatic
- SPICE takes these capacitances already into account.



# Example: inverter chain

# Simulation

\*Load the modules

```
.INCLUDE model28nm.spi
```

```
.INCLUDE inv.spi
```

\*Instantiation of the gate simulated

```
X1 In Out 1 0 inv
```

\*1.0v between Vdd and Vss

```
VCC 1 0 DC 1.0V
```

\*Simulation input

```
Vin In 0 pw1(0ns 0 3ns 0 15ns 1.0 20ns 1.0 35ns 0)
```

\*Duration of simulation (step time and total time)

```
.TRAN 1ns 35ns
```

```
.END
```

# Example: inverter

# Simulation

---

\*Load the modules

```
.INCLUDE model28nm.spi
```

```
.INCLUDE inv.spi
```

\*Instantiation of the gate simulated

```
X1 In InOut 1 0 inv  
X2 InOut Out 1 0 inv
```

\*1.0v between Vdd and Vss

```
VCC 1 0 DC 1.0V
```

\*Simulation input

```
Vin In 0 pw1(0ns 0 3ns 0 15ns 1.0 20ns 1.0 35ns 0)
```


\*Duration of simulation (step time and total time)

```
.TRAN 1ns 35ns
```

```
.END
```

# Example: inverter

# Simulation

 

# Example: complex gate

# Layout

- Function:

F


- Inputs:

A, B, C, D

- Objective:

Extract function


Parasitic capacitances

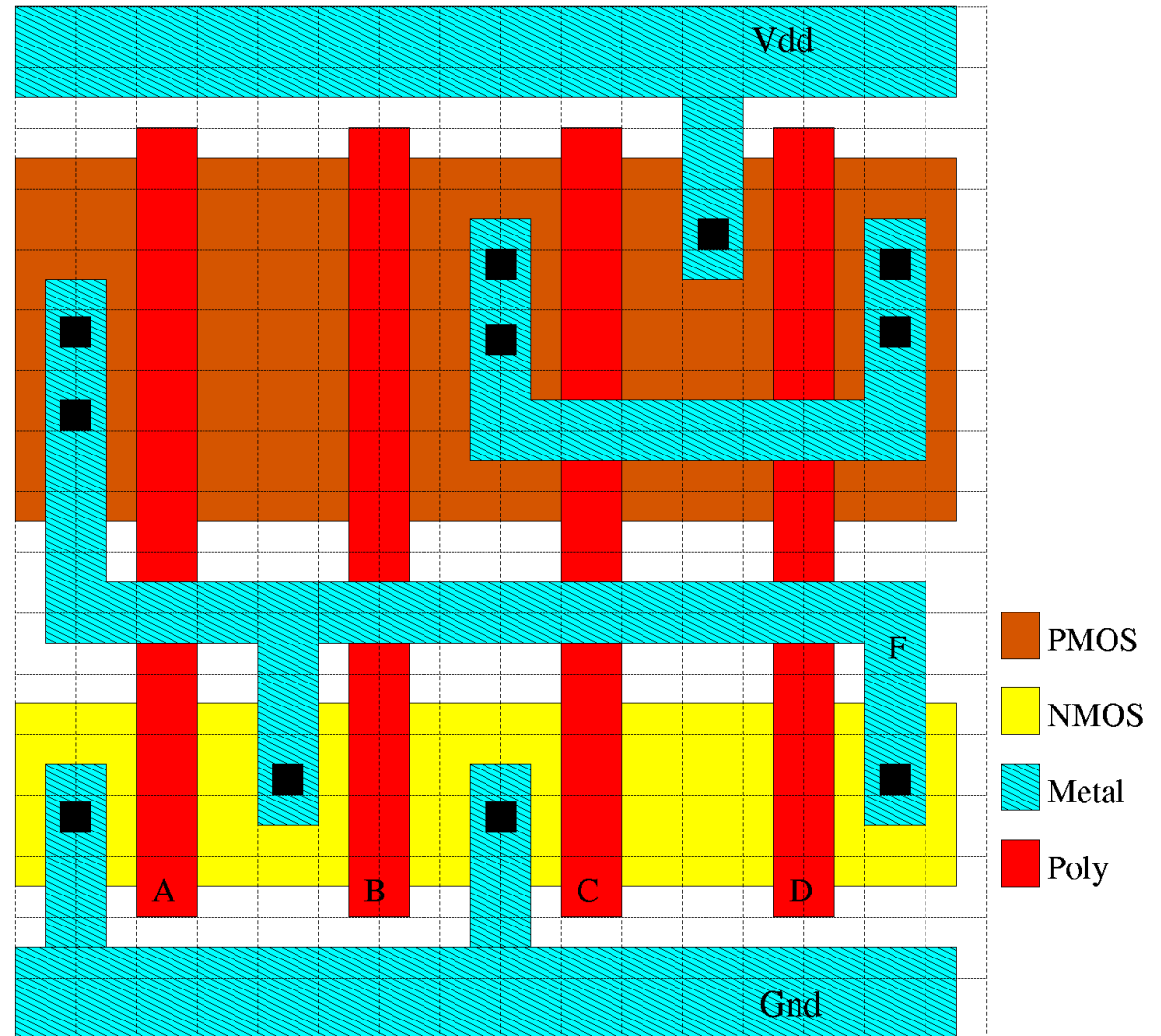
 
# Example: Brent-Kung Adder

---

- 32-bit Brent-Kung Adder:
  - Static CMOS
  - SPICE model (without connections)



# Conclusions

---

- Electric simulation of digital circuits.
- Much more detailed than logic simulators:
  - Capacitances, resistances, transistors.
  - Can model interconnections (i.e. buses).
- Large simulation times.
- No (built-in) modelling of effects such as:
  - Cross-talk
  - Power consumption / energy